

I.D. No.	
Student Name	
Batch No.	
Day & Date	

Signature of the Instructor with Date	
---------------------------------------	--

## Experiment 1

### Characterization of Op-amp

#### Objective:

To study

1. The input offset voltage
2. The input bias and offset current
3. Open loop gain
4. Slew rate

#### Components required:

IC 741, 10 k $\Omega$  Potentiometer, Resistors - 10,100,1k,1.5K,5.6k,10k,100k,and 1M  $\Omega$ .

#### Experiment:

##### 1. Input offset voltage

1.1 Assemble the circuit as shown in Figure 1, with  $R_1 = 100 \Omega$  and  $R_2 = 1k\Omega$ . Observe the dc output voltage. Calculate the input offset voltage which is given by

$$V_{os} = V_o \times R_1 / (R_1 + R_2)$$

Draw the circuit of Fig6.3 of TB2 Page No. 43

$R_2$ in $\Omega$	$V_o$ in V	$V_{os}=V_o \times R_1/(R_1+R_2)$ in V
1k		
10k		
100k		

1.2 From the data sheet of 741 op-amp, find the maximum value of input bias current,  $I_{Bmax}$ . Calculate the input offset voltage, which is given by  $I_{Bmax} \times R_1$ .

$I_{Bmax}$ =..... Input offset voltage

1.3 Compare the results of step (i) and (ii).

Parameter	From step 1.1	From step 1.2
$V_{os}$		

1.4 Connect the fixed terminals of a 10 k $\Omega$  potentiometer (nulling potentiometer) between pins 1 and 5 of the op-amp and the variable terminal to the negative power supply voltage, -15 V. Change the knob of the potentiometer to make the output zero. This nulls the effect of input offset voltage.

## 2. Input Bias current and input offset currents:

2.1 Assemble the voltage follower circuit as shown in Figure 2. Connect the non-inverting input to ground. Using a nulling potentiometer, make the output zero for zero input as per procedure 1.4.

Draw the circuit of Fig6.4 of TB2 Page No. 44

2.2 Connect a resistor  $R_1$  of value  $1\text{ M}\Omega$  between the non-inverting input and ground. Measure the output voltage  $V_{o2}$ . Calculate the current  $I_{B2}$ , given by  $I_{B2}=V_{o2}/R_1$ .

$$V_{o2} = \dots\dots\dots$$

$$I_{B2}=V_{o2}/R_1=\dots\dots\dots$$

2.3 Remove the resistor  $R_1$  and ground the non-inverting input. Now connect resistor  $R_1$  of value  $1\text{ M}\Omega$  between the inverting input and output. Measure the output voltage  $V_{o1}$ . Calculate the current  $I_{B1}$ , given by  $I_{B1}=V_{o1}/R_1$ .

$$V_{o1} = \dots\dots\dots$$

$$I_{B1}=V_{o1}/R_1=\dots\dots\dots$$

2.4 Calculate the input bias current and the input offset current from these two values.

2.5 Compare the results with the data sheet values.

Parameter	From step 2.4	From Data Sheet
Input bias current		
Input offset current		

### 3. Open-loop gain

3.1 Assemble the circuit as shown in Figure 3. Given  $R_1=1.5\text{ k}\Omega$ ,  $R_2= 5.6\text{ k}\Omega$ ,  $R_3= 10\text{ k}\Omega$  and  $R_4= 10\Omega$ .

Draw the circuit of Fig6.6 of TB2 Page No. 45

3.2 Connect a dc source at the input  $V_s$ , and adjust its value so that the output is equal to -10V. Measure  $V_1$ .

$$V_1 = \dots\dots\dots V$$

3.3 Calculate the differential input voltage  $V_{diff} = V_{II} - V_{NII} = V_1/1000$

3.4 Calculate the open-loop gain,  $A = V_o/V_{diff}$ .

#### 4. Slew Rate

4.1 Assemble the voltage follower circuit.

4.2 Apply 10Vp-p, 10 kHz square wave input,  $V_s$ .

4.3 Measure the rise time of the output waveform and calculate the slew rate.

4.4 Assemble a inverting amplifier circuit with a gain of 1, by selecting  $R_1 = R_F = 10 \text{ k}\Omega$ . Repeat steps 4.2 and 4.3.

4.5 Compare the two values.

Draw the circuit of voltage follower and inverting amplifier

Circuit	Rise time	$V_{op-p}$ in Volts	Slew Rate= $V_{op-p}/\text{rise time}$
Voltage follower			
Inverting Amplifier			

## 5 PSPICE Simulations:

Use the macro model  $\mu A$  741 and connect a load resistor of  $10\text{ k}\Omega$  and power supply voltages of  $\pm 15\text{ V}$ .

5.1 Simulate the circuit as used in experiment 1.1 using PSPICE. Do the dc analysis to print the values of the output voltage. Calculate the input offset voltage. Compare the results with the experimental results.

5.2 Simulate the circuit, as used in experiment steps 2.1 through 2.3, using PSPICE. Do the dc analysis to print the values of the output voltage. Calculate the input bias and offset currents. Compare the results with the experimental results.

5.3 Simulate the circuit, as used in experiment steps 3.1 through 3.2, using PSPICE. Compare the results with the experimental results.

## 6. Viva Questions- Answer the following:

- (a) The open loop gain of opamp 741 is \_\_\_\_\_.
- (b) The unity gain bandwidth of opamp 741 is \_\_\_\_\_.
- (c) For a good amplifier, slew rate should be very high. State true or false. \_\_\_\_
- (d) The differential input impedance of opamp 741 is \_\_\_\_\_
- (e) The CMRR of a good opamp should be as low as possible. State true or false. \_\_\_\_\_

I.D. No.	
Student Name	
Batch No.	
Day & Date	

Signature of the Instructor with Date	
---------------------------------------	--

## Experiment 2

### Inverting Amplifier, Integrator, Non-inverting Amplifier, Adder and Subtractor

#### Objective:

To design and study:

1. Inverting amplifier,
2. Integrator
3. Non-inverting amplifier
4. Adder
5. Subtractor

#### Components required:

Dual tracking power supply or  $\pm 15$  V split power supply, function generator, resistors and capacitors.

#### Experiment:

##### 1. Inverting amplifier:

1.1 Design an inverting amplifier for the gain of 15. Let  $R_1 = 1\text{k}\Omega$ . Assemble the circuit on breadboard and feed sinusoidal input signal of amplitude 100 mV and frequency 1 kHz. Observe the input and output voltages on a CRO. Determine the gain of the amplifier and phase difference between the input and output voltages.

1.2 Now vary the input signal frequency keeping the amplitude fixed and find the bandwidth. The bandwidth is equal to the higher cutoff frequency which is the frequency at which the gain reduces to 0.707 of the mid-band frequency gain.

1.3 Calculate the gain-bandwidth product.

1.4 Compare the results with the theoretical values.

$R_1 = \dots\dots\dots$  and  $R_F = \dots\dots\dots$

Draw the circuit of inverting amplifier

Input voltage,  $v_s = \dots\dots\dots$

Output voltage,  $v_o = \dots\dots\dots$

Voltage gain  $A_v = \frac{v_o}{v_s} = \frac{\dots\dots}{\dots\dots} = \dots\dots\dots$

Phase difference between input and output voltages=.....

Frequency (Hz)	Input voltage $v_s$ (V)	Output voltage $v_o$ (V)	Voltage gain, $A_v = \frac{v_o}{v_s}$	Voltage gain (dB)
500				
1k				
10k				
50k				
60k				
70k				
100k				

Higher cutoff frequency  $f_H = 0.707 A_{v(max)} = \dots\dots$

Gain bandwidth product  $GBW = A_{v(max)} \times f_H = \dots\dots\dots$

Parameter	Experimental	Theoretical
Gain		
Cut-off frequency		
Gain-bandwidth		
Phase difference		

## 2. Integrator:

Draw the circuit of integrator

2.1 Assemble an integrator with  $R = 1k\Omega$  and  $C = 0.1 \mu F$ . Connect a resistor  $R_F$  of value  $1 M\Omega$  across the capacitor. Feed 1V(peak-peak), 500 Hz




square wave input and observe input and output voltages on a CRO. Determine the gain of the amplifier. Plot the input and output voltages on the same scale.

2.2 Now change the value of  $R_F$  to  $1\text{ k}\Omega$  and repeat the observations. Explain the changes in the output.

2.3 Now change the input signal to sinusoidal input of amplitude  $1\text{V}$  and frequency  $500\text{ Hz}$  and observe the output.

Gain of the amplifier = .....

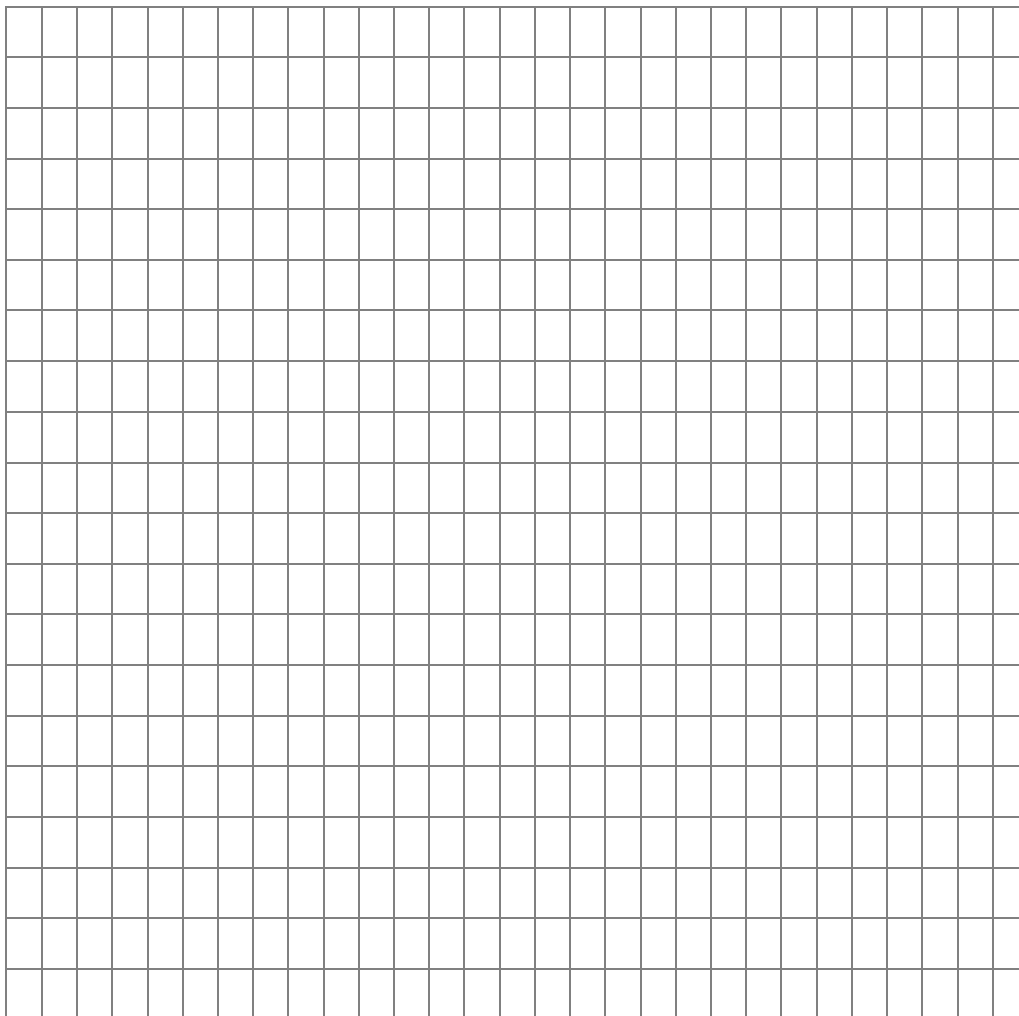

### 3. Non-Inverting amplifier:

Draw the circuit of op-amp non-inverting amplifier

1.1 Design a non-inverting amplifier for the gain of 16. Let  $R_1 = 1\text{k}\Omega$ . Assemble the circuit on breadboard and feed sinusoidal input signal of amplitude 100 mV and frequency 1 kHz. Observe the input and output voltages on a CRO. Determine the gain of the amplifier and phase difference between the input and output voltages.

1.2 Now vary the input signal frequency keeping the amplitude fixed and find the bandwidth.

1.3 Calculate the gain-bandwidth product.

1.4 Compare the results with the theoretical values.

$R_1 = \dots\dots\dots$  and  $R_F = \dots\dots\dots$ .

Input voltage,  $V_i = \dots\dots\dots$

Output voltage,  $V_o = \dots\dots\dots$

Voltage gain  $A_v = \frac{V_o}{V_s} = \frac{\dots\dots\dots}{\dots\dots\dots} = \dots\dots\dots$

Phase difference between input and output voltages =  $\dots\dots\dots$

Frequency (Hz)	Input voltage $v_s$ (V)	Output voltage $v_o$ (V)	Voltage gain, $A_v = \frac{v_o}{v_s}$	Voltage gain (dB)
500				
1k				
10k				
50k				
60k				
70k				
100k				

Higher cutoff frequency  $f_H = 0.707 A_{v(max)} = \dots\dots$

Gain bandwidth product  $GBW = A_{v(max)} \times f_H = \dots\dots\dots$

Parameter	Experimental	Theoretical
Gain		
Cut-off frequency		
Gain-bandwidth		
Phase difference		

#### 4. Adder:

2.1 Assemble an analog adder circuit with  $R_F = R_1 = 8.2 \text{ k}\Omega$ ,  $R_2 = 3.9 \text{ k}\Omega$  and  $R_3 = 2 \text{ k}\Omega$ . Feed sinusoidal input of amplitude 1 V and frequency 1 kHz to each input. Measure the amplitude of the output voltage and compare with the theoretical values.

2.2 Compare the experimental results with the theoretical values.

Draw the circuit of op-amp adder

$$\text{Output voltage, } v_o = - \left[ \left( \frac{R_F}{R_1} \right) v_1 + \left( \frac{R_F}{R_2} \right) v_2 + \left( \frac{R_F}{R_3} \right) v_3 \right]$$

$$= \dots\dots\dots$$

$R_F = R_1 = 8.2 \text{ k}\Omega$ ,  $R_2 = 3.9 \text{ k}\Omega$  and  $R_3 = 2 \text{ k}\Omega$

$v_1 = v_2 = v_3 = 1 \text{ V}$  and frequency = 1 kHz

Thus  $v_o = \dots\dots\dots$

Experimental value of  $v_o = \dots\dots$

#### 5. Subtractor:

Draw the circuit of op-amp subtractor

3.1 Assemble a subtractor circuit with  $R_F = R_1 = 8.2 \text{ k}\Omega$ . Feed  $V_1 = 2 \text{ V}$  and  $V_2 = 0.5 \text{ V}$  sinusoidal signal of frequency  $1 \text{ kHz}$ . Observe the input and output voltages on a CRO. To get two signals from the same source, use a high resistance potentiometer.

3.2 Plot  $v_1$ ,  $v_2$  and  $v_o$  on the same scale. Compare the amplitudes with the theoretical values.


$R_F = R_1 = 8.2 \text{ k}\Omega$ .

$v_1 = 2 \text{ V}$  and  $v_2 = 0.5 \text{ V}$  sinusoidal signal of frequency  $1 \text{ kHz}$ .

Theoretical value of output voltage =  $\frac{R_F}{R_1}(v_2 - v_1) = \dots\dots\dots$

Measured output voltage

$v_o = \dots\dots\dots \text{V}$

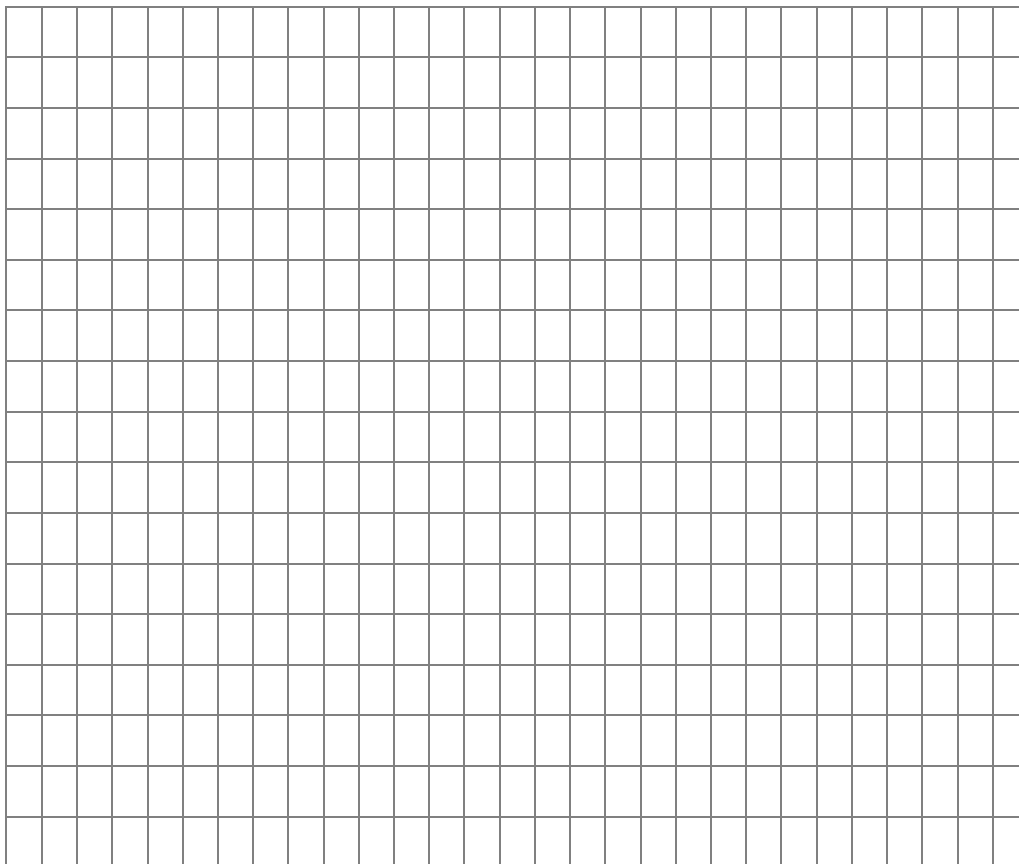

6.

**PSPICE Simulation:**

Use the macro model  $\mu A$  741 and connect a load resistor of  $10\text{ k}\Omega$  and power supply voltages of  $\pm 15\text{ V}$ .

6.1 Simulate the Differentiator circuit with  $R=10\text{ k}\Omega$  and  $C=0.05\text{ }\mu\text{F}$  as used in experiment 4.1 using PSPICE. Plot the input and output voltages on the same scale. Determine the positive and negative peak voltages of the output. Also determine the rise and fall times of the output voltage. Assume  $\pm 0.1\text{ V}$ ,  $5\text{ kHz}$  triangular wave input.

6.2 Simulate the non-inverting amplifier circuit (for the gain of 16), as used in experiment step 5.1 using PSPICE. Assume sinusoidal input of amplitude  $100\text{ mV}$  and frequency  $1\text{ kHz}$ . Find the gain of the circuit and phase difference between the input and output voltages. Plot the frequency response curve of the amplifier and find the bandwidth. Compare the results with the experimental results.

6.3 Simulate the voltage follower circuit, as used in experiment step 6.1 using PSPICE. Assume sinusoidal input of amplitude  $100\text{ mV}$  and frequency  $1\text{ kHz}$ . Find the gain of the circuit and phase difference between the input and output voltages. Plot the frequency response curve of the amplifier and find the bandwidth. Compare the results with the non-inverting amplifier.

#### 6. Quiz Questions:

- (a) The minimum voltage gain possible for an non-inverting amplifier is \_\_\_\_\_
- (b) With  $\pm 15\text{ V}$  supply voltage, the maximum rail to rail voltage swing of an inverting amplifier is \_\_\_\_\_.
- (c) The opamp in an inverting amplifier operates in \_\_\_\_\_ region.
- (d) If the gain of an inverting amplifying circuit is 10 and  $\pm 15\text{ V}$  power supplies are used. What range of input values allows the opamp to be in linear region?  
\_\_\_\_\_V.